

Final Review

Unit 11 - Dc Circuits

- (53) energy source (^{usually} battery), continuous loop,
device to use energy (resistor, lightbulb, etc.)
- (54) voltage \rightarrow volts (V)
current \rightarrow amps (A)
resistance \rightarrow ohms (Ω)
- (55) $I = Q/t = 8.4/10 = \boxed{0.84 \text{ A}}$
- (56) $I = Q/t \rightarrow Q = I \cdot t = (2.5)(3) = \boxed{7.5 \text{ C}}$
- (57) $I = \frac{V}{R}$ so as voltage \uparrow , current ~~also~~ increases
- (58) $I = \frac{V}{R}$ so as $R \uparrow$, current decreases
- (59) $I = \frac{V}{R} = 12/6 = \boxed{2 \text{ A}}$
- (60) $V = IR \rightarrow 6 = 12 \cdot R \rightarrow \boxed{R = 0.5 \Omega}$
- (61) current is the same across each resistor in series
- (62) voltage drop is the same across resistors in parallel
- (63) a) $R_s = 3 + 2 + 7 = \boxed{12 \Omega}$
b) $I = \frac{V}{R} = 24/12 = \boxed{2 \text{ A}}$
c) $I = 2 \text{ A}$
d) $V_{3\Omega} = 2(3) = \boxed{6 \text{ V}}$
 $V_{2\Omega} = 2(2) = \boxed{4 \text{ V}}$
 $V_{7\Omega} = 2(7) = \boxed{14 \text{ V}}$
- (64) a) $\frac{1}{R_p} = \frac{1}{4} + \frac{1}{5} + \frac{1}{10} = \frac{11}{20} \rightarrow R_p = \frac{20}{11} = \boxed{1.82 \Omega}$
b) $I = \frac{V}{R} = 6/1.82 = \boxed{3.3 \text{ A}}$
c) $V = \boxed{6 \text{ V}}$ across each
d) $I_{4\Omega} = \frac{6}{4} = \boxed{1.5 \text{ A}}$
 $I_{5\Omega} = \frac{6}{5} = \boxed{1.2 \text{ A}}$
 $I_{10\Omega} = \frac{6}{10} = \boxed{0.6 \text{ A}}$